

Digital Systems II - DGD 4

TA Office hours
SITE 2021 - 11-1 PM

Incomplete assignments

- According to VHDL code only IF and THEN is required.

Example

According to the following code:

```
process(a,b)
Begin
    If (a=b) then
        Eq <= '1';
    End if
End process
```

Eq will only be one if a = b.

Any other cases will make EQ retain the original value of EQ.

Fixed:

```
process(a,b)
Begin
    If (a=b) then
        Eq <= '1';
    Else
        Eq <= '0';
    End if
End process
```

Another example

```
process(a,b)
begin
    if (a>b) then
        gt <= '1';
    elsif (a=b) then
        eq <= '1';
    else
        lt <= '1';
    end if
end process
```


Fixed:

```
process(a,b)
begin
    gt <= '0';
    lt <= '0';
    eq <= '0';
    if (a>b) then
        gt <= '1';
    elsif (a=b) then
        eq <= '1';
    else
        lt <= '1';
    end if
end process
```

Question 1

Draw the conceptual diagram of:

```
3  if (a > b and op="00") then
4      y <= a - b;
5      z <= a - 1;
6      status <= '0';
7  else
8      y <= b - a;
9      z <= b - 1;
10     status <= '1';
11 end if;
12
```

 

Question 2

Consider the code:

```
3  if (a > b) then
4      y <= a - b;
5  else
6      if(a > c)
7          y <= a - c;
8      else
9          y <= a + 1;
10     end if;
11 end if;
```

Rewrite the code using two concurrent conditional signal assignments:

```
signal temp1, temp2 : std_logic
temp1 <= (a-c) when (a>c) else (a+1);
y <= (a-b) when (a>b) else temp1
```

Rewrite it with one concurrent conditional statement:

```
signal temp1, temp2 : std_logic
y <= (a-b) when (a>b) else (a-c) when (a>c) else (a+1);
```


Rewrite using a case statement:

```
temp1 <= '1' when a>b else '0';
temp2 <= '1' when a>c else '0';
```

```
case(temp1&temp2) is
    when "00" =>
        y <= a+1;
    when "01" =>
        y <= a-c;
    when "10" =>
        y <= a-b;
    when others =>
        y <= a-b;
end case
```

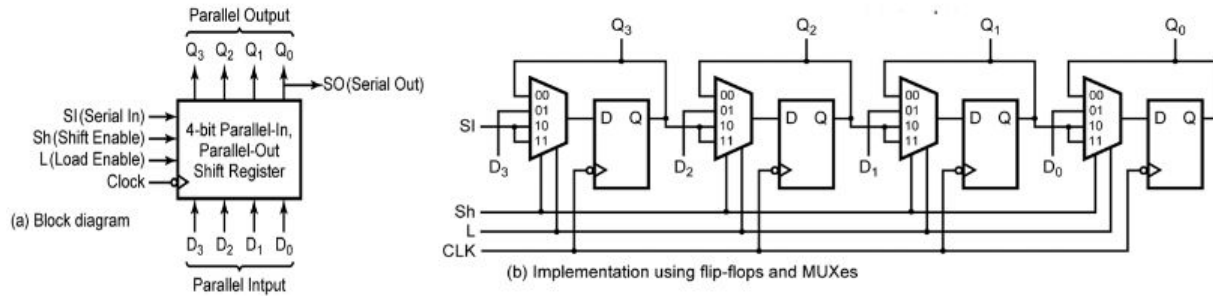Question 7

The following figure shows a parallel-in parallel out right shift register, Part a is the block diagram and part b is the implementation using flip flops and multiplexers



| Inputs | | Next State | | | | Action |
|------------|-----------|------------|---------|---------|---------|-------------|
| Sh (Shift) | Ld (Load) | Q_3^+ | Q_2^+ | Q_1^+ | Q_0^+ | |
| 0 | 0 | Q_3 | Q_2 | Q_1 | Q_0 | no change |
| 0 | 1 | D_3 | D_2 | D_1 | D_0 | load |
| 1 | X | SI | Q_3 | Q_2 | Q_1 | right shift |