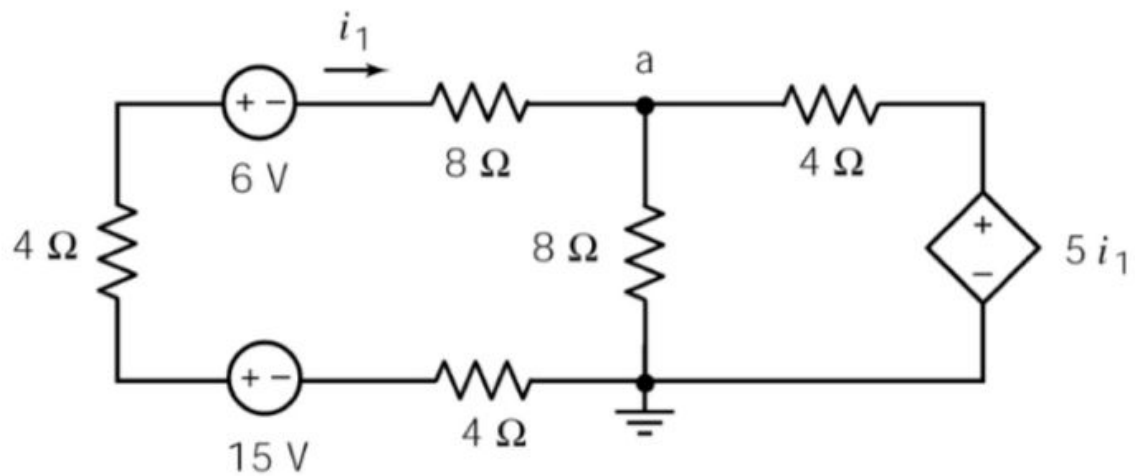


Assignment 1



Considering the circuit shown above.

Determine the power supplied/received by each element in the circuit.